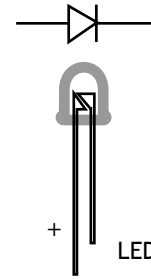
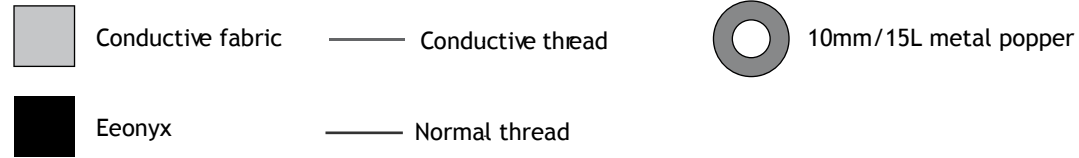


# Fabric Potentiometer + LED circuit

Made from: stretch conductive fabric, conductive thread, fusible interfacing, Eeonyx, LED, 2 set of poppers, neoprene

Necessary components: Double AA battery pouch, 2 AA batteries



[www.KOBAKANT.at](http://www.KOBAKANT.at)

