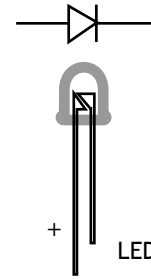


Fabric Potentiometer (circle) + LED circuit

Made from: stretch conductive fabric, conductive thread, fusible interfacing, Eeonyx, LED, 2 set of poppers, neoprene

Necessary components: Double AA battery pouch, 2 AA batteries

- Conductive fabric
- Conductive thread
- 10mm/15L metal popper
- Eeonyx
- Normal thread
- metal wire



www.KOBAKANT.at

